

Verilog Implementation and Analysis of Adder Architectures

June 1, 2025

SUBMITTED BY

SREENESH K.S¹

Rajagiri School of Engineering & Technology (RSET)

¹u2201199@rajagiri.edu.in

Contents

| | | |
|---|----------------------------------|----|
| 1 | Introduction | 3 |
| 2 | Simulation and Synthesis Setup | 3 |
| 3 | Timing Analysis | 3 |
| 4 | Power Analysis | 3 |
| 5 | Resource Utilization | 4 |
| 6 | Result Comparison | 4 |
| 7 | Proof Regarding above statements | 5 |
| 8 | Conclusion | 29 |

1 Introduction

This project involves the design and implementation of various adder architectures using Verilog HDL. The designs were synthesized and analyzed based on timing, power consumption, and Area utilization. The architectures considered include:

- 4 Bit Ripple Carry Adder (RCA)
- 4 Bit Carry Lookahead Adder (CLA)
- 4 Bit Carry Skip Adder (CSKA)
- 4 Bit Carry Select Adder (CSA)

2 Simulation and Synthesis Setup

- Clock Period: 10 ns
- Tools Used: Vivado

3 Timing Analysis

Table 1: Timing Summary

| Adder Type | Worst Negative Slack (ns) | Hold Slack (ns) | Delay (ns) |
|-----------------------|---------------------------|-----------------|------------|
| Ripple Carry Adder | 7.812 | 0.208 | 2.188 |
| Carry Lookahead Adder | 8.282 | 0.123 | 1.718 |
| Carry Skip Adder | 7.931 | 0.149 | 2.069 |
| Carry Select Adder | 8.083 | 0.131 | 1.917 |

Inference: Carry Lookahead adder [CLA] has the most positive WNS i.e., the shortest critical path delay Ripple carry adder is the slowest

SLACK= Required Time-Arrival Time

4 Power Analysis

Table 2: Power Summary

| Adder Type | On-Chip Power (W) | Device Static Power (W) | Dynamic Power |
|-----------------------|-------------------|-------------------------|---------------|
| Ripple Carry Adder | 0.074 | 0.070 | 0.003 |
| Carry Lookahead Adder | 0.115 | 0.112 | 0.004 |
| Carry Skip Adder | 0.074 | 0.070 | 0.003 |
| Carry Select Adder | 0.088 | 0.081 | 0.007 |

Inference: For **Ripple Carry Adder** [RCA] due to low transistor count and minimal hardware power consumption.

For the **Carry Skip adder**, as it optimizes carry propagation by skipping blocks when possible and power consumption is usually similar to or higher than RCA but less than CLA & CSA ,as 4bit the powerconsumption is slightly similar to RCA

For **Carry Lookahead adder** , Transistor count is high and generate carry signals in parallel. Therefore higher power consumption

For **carry select adder** the hardware is not minimal therefore it consumes more power due to duplicated hardware and parallel operation as per theoretical background. but after syntesis it gives less power consumption maybe because of less bit used.

5 Resource Utilization

Table 3: Utilization Summary

| Adder Type | Slice LUTs | Slice Registers | Bonded IOBs |
|-----------------------|------------|-----------------|-------------|
| Ripple Carry Adder | 5 | 14 | 16 |
| Carry Lookahead Adder | 6 | 14 | 16 |
| Carry Skip Adder | 6 | 14 | 16 |
| Carry Select Adder | 11 | 14 | 16 |

Inference: The Ripple Carry Adder uses the fewest LUTs (5), making it the most area-efficient. Carry Select Adder uses the most LUTs (11) due to parallel computation blocks and multiplexers. All architectures use the same number of registers (14) and IOBs (16), indicating that differences lie mainly in combinational logic, not in I/O or sequential elements.

6 Result Comparison

The performance of the four 4-bit adder architectures—Ripple Carry Adder (RCA), Carry Lookahead Adder (CLA), Carry Skip Adder (CSKA), and Carry Select Adder (CSA)—is compared based on three major parameters: **timing**, **power consumption**, and **resource utilization**.

Timing Performance:

The **Carry Lookahead Adder (CLA)** has the lowest delay (1.718 ns), making it the fastest among the four. This is due to its parallel carry generation logic, which minimizes the critical path delay.

Power Consumption:

The **Ripple Carry Adder (RCA)** and **Carry Skip Adder (CSKA)** consume the least dynamic power (0.003 W) due to their simpler structures and minimal switching activity in a small 4-bit implementation.

The **Carry Select Adder (CSA)**, despite its theoretical complexity, consumes slightly more dynamic power due to parallel operations. However, in this 4-bit design, the power is still relatively low.

Resource Utilization:

The **Ripple Carry Adder** uses the fewest LUTs (5), indicating high area efficiency.

The **Carry Select Adder** uses the most LUTs (11) due to duplicated logic blocks and multiplexers, making it the least area-efficient among the four.

Conclusion:

For **low-power and area-efficient** designs, especially in low-bit applications, **RCA** or **CSKA** is preferable.

For **high-speed operations**, **CLA** is ideal, despite slightly higher power and area usage.

CSA, while theoretically faster in higher bit-widths, shows higher resource consumption with no significant timing benefit in the 4-bit range, and is less efficient in this case.

 


Figure 1: Comparison of 4-bit Adder Architectures

7 Proof Regarding above statements

RIPPLE CARRY ADDER REPORT

RIPPLE CARRY ADDER CODE:

```
Project Summary x dff_single.v x d_flip_flop.v x FULL_ADDER_4BIT.v * x TOP_MODULE.v x
K:/XILINX/INTERNSHIP_DAY_2/INTERNSHIP_DAY_2.srscs/sources_1/new/FULL_ADDER_4BIT.v
Q [Icons]
1 module FULL_ADDER_4BIT(sum,c_out,a,b,c_in,c1,c2,c3);
2   input [3:0]a,b;
3   input c_in;
4   output c_out;
5   output c1,c2,c3;
6   output [3:0]sum;
7   FULL_ADDER FA1(sum[0],c1,a[0],b[0],c_in);
8   FULL_ADDER FA2(sum[1],c2,a[1],b[1],c1);
9   FULL_ADDER FA3(sum[2],c3,a[2],b[2],c2);
10  FULL_ADDER FA4(sum[3],c_out,a[3],b[3],c3);
11 endmodule
12
13 module FULL_ADDER(sum,c_out,a,b,c_in);
14   input a,b,c_in;
15   output reg sum,c_out;
16
17   always @(*)
18   begin
19     sum=a^b^c_in;
20     c_out=(a&b) | (b&c_in) | (a&c_in);
21   end
22 endmodule
```

TESTBENCH:

```
x FULL_ADDER_4BIT.v x TOP_MODULE.v x FULL_ADDER_4BIT_TB.v x Untitled 1*
K:/XILINX/INTERNSHIP_DAY_2/INTERNSHIP_DAY_2.srscs/sim_1/new/FULL_ADDER_4BIT_TB.v
Q [Icons]
1 `timescale 1ns / 1ps
2 module FULL_ADDER_4BIT_TB;
3   reg [3:0] a, b;
4   reg c_in;
5   wire [3:0] sum;
6   wire c_out;
7   wire c1, c2, c3;
8
9   FULL_ADDER_4BIT dut (.sum(sum),.c_out(c_out),.a(a),
10    .b(b),.c_in(c_in),.c1(c1),.c2(c2),.c3(c3));
11   initial begin
12     a = 4'b1011; b = 4'b0100; c_in = 0; #10;
13     a = 4'b0011; b = 4'b1000; c_in = 1; #10;
14     $finish;
15   end
16 endmodule
17
```

ONE BIT D FLIPFLOP:

Project Summary × dff_single.v × d_flip_flop.v × FULL_ADDER_4BIT.v * × TOP

K:/XILINX/INTERNSHIP_DAY_2/INTERNSHIP_DAY_2.srcs/sources_1/new/dff_single.v

Q

📁

↶

↷

✂

📄

📄

✖

//

📊

💡

```
1 module D_FF_1BIT (input clk,reset,d,
2     output reg q, qb );
3     always @(posedge clk or posedge reset)
4     begin
5         if (reset)
6         begin
7             q <= 1'b0;
8             qb<=1'b1;
9         end
10        else
11        begin
12            q <= d;
13            qb <= ~d;
14        end
15    end
16
17 endmodule
```


FOUR BIT D FLIPFLOP:

```
Project Summary x dff_single.v x d_flip_flop.v x FULL_ADDER_4BIT.v * x T
K:/XILINX/INTERNSHIP_DAY_2/INTERNSHIP_DAY_2.srscs/sources_1/new/d_flip_flop.v

Q [Icons]

1 module D_FF_4BIT (input clk,reset,[3:0] d,
2                   output reg [3:0] q,qb );
3
4 always @(posedge clk or posedge reset)
5 begin
6     if (reset)
7     begin
8         q <= 4'b0000;
9         qb<=4'b1111; // Reset output to 0
10        end
11    else
12    begin
13        q <= d;
14        qb <= ~d;
15    end
16 end
17 endmodule
18
19
20
```

WAVEFORM:

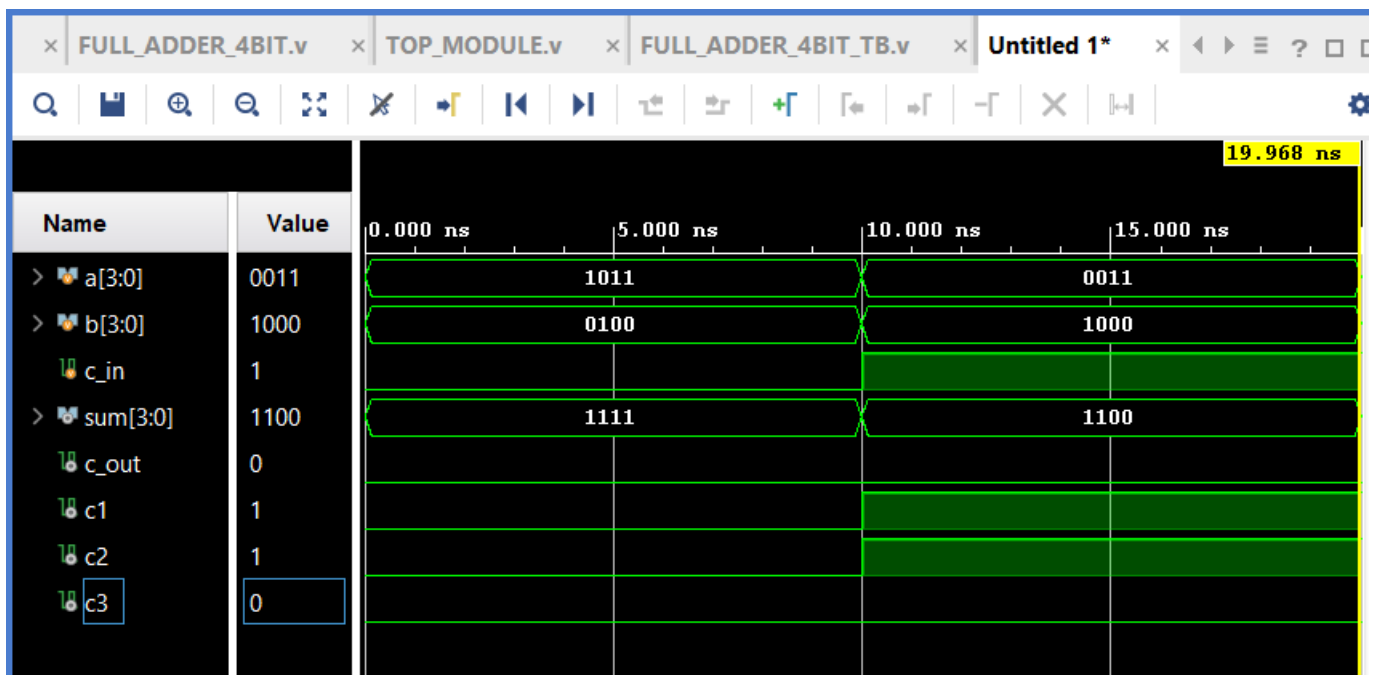

TOP MODULE :

```
Project Summary x dff_single.v x d_flip_flop.v x FULL_ADDER_4BIT.v x TOP_MODULE.v x
K:/XILINX/INTERNSHIP_DAY_2/INTERNSHIP_DAY_2.srcs/sources_1/new/TOP_MODULE.v

1 module fourtop(a_in, b_in, cin_in, clk, clear, sum_out, cout_out);
2     input [3:0] a_in, b_in;
3     input cin_in, clk, clear;
4     output [3:0] sum_out;
5     output cout_out;
6
7     wire [3:0] a, b, sum;
8     wire c_in, c_out;
9     wire [3:0] a_bar, b_bar, sum_bar;
10    wire cin_bar, cout_bar;
11
12    D_FF_4BIT dff_a(clk, clear, a_in, a, a_bar);
13    D_FF_4BIT dff_b(clk, clear, b_in, b, b_bar);
14    D_FF_1BIT dff_c(clk, clear, cin_in, cin, cin_bar);
15
16    FULL_ADDER_4BIT FA(sum, cout, a, b, cin);
17
18    D_FF_4BIT dff_sum(clk, clear, sum, sum_out, sum_bar);
19    D_FF_1BIT dff_cout(clk, clear, cout, cout_out, cout_bar);
20 endmodule
21
```


UTILIZATION AREA SUMMARY:

Q ≡ ⚙ % Hierarchy

| Name | 1 | Slice LUTs (32600) | Slice Registers (65200) | Bonded IOB (210) | BUFGCTRL (32) |
|--------------------------|---|-----------------------|----------------------------|---------------------|------------------|
| ▼ N fourtop | | 4 | 14 | 16 | 1 |
| I dff_a (D_FF_4BIT) | | 0 | 4 | 0 | 0 |
| I dff_b (D_FF_4BIT_0) | | 4 | 4 | 0 | 0 |
| I dff_c (D_FF_1BIT) | | 0 | 1 | 0 | 0 |
| I dff_cout (D_FF_1BIT_1) | | 0 | 1 | 0 | 0 |
| I dff_sum (D_FF_4BIT_2) | | 0 | 4 | 0 | 0 |

DESIGN TIMING REPORT:

| Setup | Hold | Pulse Width |
|--------------------------------------|----------------------------------|---|
| Worst Negative Slack (WNS): 7.812 ns | Worst Hold Slack (WHS): 0.208 ns | Worst Pulse Width Slack (WPWS): 4.500 ns |
| Total Negative Slack (TNS): 0.000 ns | Total Hold Slack (THS): 0.000 ns | Total Pulse Width Negative Slack (TPWS): 0.000 ns |
| Number of Failing Endpoints: 0 | Number of Failing Endpoints: 0 | Number of Failing Endpoints: 0 |
| Total Number of Endpoints: 5 | Total Number of Endpoints: 5 | Total Number of Endpoints: 15 |

All user specified timing constraints are met.

TIMING CONSTRAINTS:

dff_single.v × d_flip_flop.v × FULL_ADDER_4BIT.v × TOP_MODULE.v × Schematic × Timing Constraints ×

≡ ⚙ ⚡ +

Create Clock

▼ Clocks (1)

Create Clock (1)

Create Generated Clock

Rename Auto-Derived C


| Position | Clock Name | Period (ns) | Rise At (ns) | Fall At (ns) | Add Clock | Source Objects | Source File | Scope |
|----------|------------|-------------|--------------|--------------|--------------------------|----------------|-------------|-------|
| 1 | clk | 10.000 | 0.000 | 5.000 | <input type="checkbox"/> | clk | <unsaved co | |

Double click to create a Create Clock constraint

CHECK TIMING :

| Unconstrained Paths - NONE - clk | |
|----------------------------------|-----------------|
| Group Name: (none) | |
| From Clock: | |
| To Clock: | clk |
| Statistics | |
| Type | Total Endpoints |
| Max Delay | 23 |
| Min Delay | 23 |

POWER REPORT:
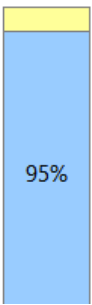
| | | | |
|--|---------------|--|------------------------------|
| Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis. | | On-Chip Power | |
| Total On-Chip Power: | 0.074 W |  | Dynamic: 0.003 W (5%) |
| Design Power Budget: | Not Specified | | 13% Clocks: <0.001 W (13%) |
| Process: | typical | | 3% Signals: <0.001 W (3%) |
| Power Budget Margin: | N/A | | 1% Logic: <0.001 W (1%) |
| Junction Temperature: | 25.4°C | | 83% I/O: 0.003 W (83%) |
| | | | Device Static: 0.070 W (95%) |

CARRY LOOK AHEAD ADDER REPORT

Submitted by SREENESH K.S

RAJAGIRI SCHOOL OF ENGINEERING & TECHNOLOGY [RSET]

MAIL ID : SREENESH K S RSET u2201199@rajagiri.edu.in

CODE

```
module carrylook(a,b,cin,s,cout);
    input [3:0]a,b;
    input cin;
    output [3:0]s;
    output cout;
    wire [3:0]p,g,c;
) assign p[0]=a[0]^b[0];
    assign p[1]=a[1]^b[1];
    assign p[2]=a[2]^b[2];
    assign p[3]=a[3]^b[3];
    assign g[0]=a[0]&b[0];
    assign g[1]=a[1]&b[1];
    assign g[2]=a[2]&b[2];
    assign g[3]=a[3]&b[3];
    assign c[0]=g[0] | (p[0]&cin);
    assign c[1]=g[1] | (p[1]&g[0]) | (p[1]&p[0]&cin);
    assign c[2]=g[2] | (p[2]&g[1]) | (p[2]&p[1]&g[0]) | (p[2]&p[1]&p[0]&cin);
    assign c[3]=g[3] | (p[3]&g[2]) | (p[3]&p[2]&g[1]) | (p[3]&p[2]&p[1]&g[0]) | (p[3]&p[2]&p[1]&p[0]&cin);
    assign s[0]=p[0]^cin;
    assign s[1]=p[1]^c[0];
    assign s[2]=p[2]^c[1];
    assign s[3]=p[3]^c[2];

    assign cout=c[3];
endmodule
```

TESTBENCH

```
module carrylookaheadtb();
  reg [3:0] a,b;
  reg cin;
  wire [3:0] s;
  wire cout;
  carrylook dut(.a(a),.b(b),.cin(cin),.s(s),.cout(cout));
  initial begin
    a=4'b0000;
    b=4'b0000;
    cin=1'b0;
  end
  always #2 a=a+1'b1;
  always #4 b=b+1'b1;
endmodule
```

1 & 4 BIT D FLIP FLOP


```
module dffp(d,clk,clear,q,qbar);
  input d,clk,clear;
  output reg q,qbar;
  always @(posedge clk or negedge clear)
    if (clear==1'b0)
      begin
        q<=1'b0;
        qbar<=1'b1;
      end
    else
      begin
        q=d;
        qbar=~d;
      end
endmodule
```

```

) module fourbitdffp(d,clk,clear,q,qbar);
  input [3:0]d;
  input clk,clear;
  output reg [3:0]q,qbar;
) always @(posedge clk or negedge clear)
) if (clear==1'b0)
) begin
  q<=4'b0000;
  qbar<=4'b1111;
) end
  else
) begin
  q=d;
  qbar=~d;
) end
) endmodule

```

SIMULATION RESULT

 

TOP MODULE

```
module topmodule(a_in, b_in, cin_in, clk, clear, sum_out, cout_out);
    input [3:0] a_in, b_in;
    input cin_in, clk, clear;
    output [3:0] sum_out;
    output cout_out;

    wire [3:0] a, b, sum;
    wire cin, cout;

    wire [3:0] a_bar, b_bar, sum_bar;
    wire cin_bar, cout_bar;

    fourbitdffp dff_a(a_in, clk, clear, a, a_bar); //4bit dffp d=ain q=a qbar=abar
    fourbitdffp dff_b(b_in, clk, clear, b, b_bar);
    dffp dff_cin(cin_in, clk, clear, cin, cin_bar);

    carrylook FA1(a, b, cin, sum, cout);

    // Output D Flip-Flops
    fourbitdffp dff_sum(sum, clk, clear, sum_out, sum_bar);
    dffp dff_cout(cout, clk, clear, cout_out, cout_bar);

endmodule
```

UTILIZATION AREA SUMMARY

hierarchy

| Name | 1 | Slice LUTs (101400) | Slice Registers (202800) | Slice (25350) | LUT as Logic (101400) | Bonded IOB (285) | BUFGCTRL (32) |
|-------------------------|---|------------------------|-----------------------------|------------------|--------------------------|---------------------|------------------|
| topmodule1 | | 6 | 14 | 2 | 6 | 16 | 1 |
| dff_a (fourbitdffp) | | 2 | 4 | 2 | 2 | 0 | 0 |
| dff_b (fourbitdffp_0) | | 3 | 4 | 2 | 3 | 0 | 0 |
| dff_cin (dffp) | | 1 | 1 | 1 | 1 | 0 | 0 |
| dff_cout (dffp_1) | | 0 | 1 | 1 | 0 | 0 | 0 |
| dff_sum (fourbitdffp_2) | | 0 | 4 | 2 | 0 | 0 | 0 |

TIMING REPORT

WORST NEGATIVE SLACK IS 8.282ns

Tcl ConsoleMessagesLogReportsDesign RunsPowerMethodologyDRCTiming xUtilization

Q⏏⏏⏏⏏⏏⏏

Design Timing Summary

General Information

Timer Settings

Design Timing Summary

Clock Summary (1)

Methodology Summary (14)

Check Timing (15)

Intra-Clock Paths

Inter-Clock Paths

Other Path Groups

Setup

Worst Negative Slack (WNS): 8.282 ns

Total Negative Slack (TNS): 0.000 ns

Number of Failing Endpoints: 0

Total Number of Endpoints: 5

Hold

Worst Hold Slack (WHS): 0.123 ns

Total Hold Slack (THS): 0.000 ns

Number of Failing Endpoints: 0

Total Number of Endpoints: 5

Pulse Width

Worst Pulse Width Slack (WPWS): 4.600 ns

Total Pulse Width Negative Slack (TPWS): 0.000 ns

Number of Failing Endpoints: 0

Total Number of Endpoints: 15

All user specified timing constraints are met.

| Position | Clock Name | Period (ns) | Rise At (ns) | Fall At (ns) | Add Clock | Source Objects |
|----------|------------|-------------|--------------|--------------|-------------------------------------|----------------|
| 1 | clk | 10.000 | 0.000 | 5.000 | <input checked="" type="checkbox"/> | clk |

Double click to create a Create Clock constraint

Intra clock path

| Intra-Clock Paths | | | | | | | | | | | | | |
|-------------------|-------------|----------|----------|-------------------------|-----------------------|-------------|----------|----------|-------------------------|-----------------------|-----------|-----------|--------------------------|
| Clock | Edges (WNS) | WNS (ns) | TNS (ns) | Failing Endpoints (TNS) | Total Endpoints (TNS) | Edges (WHS) | WHS (ns) | THS (ns) | Failing Endpoints (THS) | Total Endpoints (THS) | WPWS (ns) | TPWS (ns) | Failing Endpoints (TPWS) |
| clk | rise - rise | 8.282 | 0.000 | 0 | 5 | rise - rise | 0.123 | 0.000 | 0 | 5 | 4.600 | 0.000 | |

Group Name: (none)

From Clock:

To Clock: clk

Statistics

| Type | Total Endpoints |
|-----------|-----------------|
| Max Delay | 37 |
| Min Delay | 37 |

Check Timing


| Timing Check | Count ▼ 1 | Worst Severity |
|----------------------------------|------------------------|----------------|
| no_input_delay | 10 | High |
| no_output_delay | 5 | High |
| no_clock | 0 | |
| constant_clock | 0 | |
| pulse_width_clock | 0 | |
| unconstrained_internal_endpoints | 0 | |
| multiple_clock | 0 | |
| generated_clocks | 0 | |
| loops | 0 | |
| partial_input_delay | 0 | |

POWER REPORTS

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.115 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 25.3°C

On-Chip Power

 

CARRY SKIP ADDER


Submitted by: Jenet Joseph

Mail ID: jenetjoseph.2004@gmail.com

CARRY SKIP ADDER CODE:

```
Project Summary x carrieskip.v x ripplecarryadder.v x fulladder.v x mux2by1.v x propg.v x
C:/Users/jenet/projectinternshipfinal/projectinternshipfinal.srscs/sources_1/new/carrieskip.v
Q [ Save Undo Redo Cut Copy Paste Delete Comment Toggle Breakpoint Toggle Lightbulb
22
23 module carrieskip(a,b,cin,sum,cout);
24
25 input [3:0] a,b;
26 input cin;
27 output [3:0] sum;
28 output cout;
29 wire [3:0] p;
30 wire c0;
31 wire bp;
32
33 ripplecarryadder rca1(.a(a[3:0]),.b(b[3:0]),.cin(cin),.sum(sum[3:0]),.cout(c0));
34 propg p1(a,b,p,bp);
35 mux2by1 m1(.I0(c0),.I1(cin),.sel(bp),.out(cout));
36
37 endmodule
38
```

WAVEFORM:

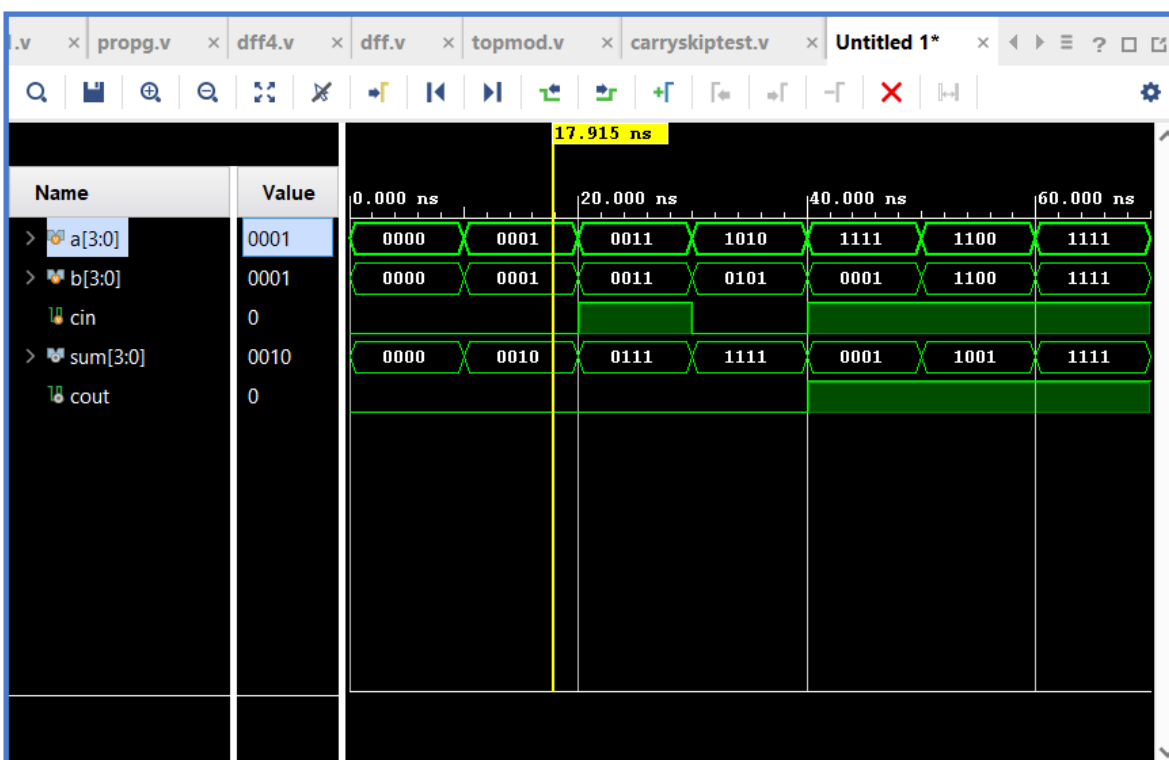

RIPPLE CARRY ADDER:

Project Summary x carryskip.v x ripplecarryadder.v x fulladder.v x mux2by1.v x propg.v x

C:/Users/jenet/projectinternshipfinal/projectinternshipfinal.srscs/sources_1/new/ripplecarryadder.v

```
23 module ripplecarryadder(a,b,cin,sum,cout);
24
25 input [3:0]a,b;
26 input cin;
27 output[3:0] sum;
28 output cout;
29 wire c1,c2,c3;
30
31 fulladder fa0(a[0],b[0],cin,sum[0],c1);
32 fulladder fa1(a[1],b[1],c1,sum[1],c2);
33 fulladder fa2(a[2],b[2],c2,sum[2],c3);
34 fulladder fa3(a[3],b[3],c3,sum[3],cout);
35
36 endmodule
37
```

FULL ADDER:

Project Summary x carryskip.v x ripplecarryadder.v x fulladder.v x mux2by1.v x propg.v x

C:/Users/jenet/projectinternshipfinal/projectinternshipfinal.srscs/sources_1/new/fulladder.v

```
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21
22 module fulladder(a,b,cin,sum,cout);
23
24 input a,b,cin;
25 output sum,cout;
26
27 assign sum=a^b^cin;
28 assign cout=(a&b) | (b&cin) | (cin&a);
29
30 endmodule
```

PROPAGATE:

Project Summary x carryskip.v x ripplecarryadder.v x fulladder.v x mux2by1.v x propg.v x

C:/Users/jenet/projectinternshipfinal/projectinternshipfinal.srscs/sources_1/new/propg.v

```
20 ///////////////////////////////////////////////////////////////////
21
22 module propg(a,b,p,bp);
23
24 input [3:0] a,b;
25 output [3:0] p;
26 output bp;
27
28 assign p= a^b;
29 assign bp= &p;
30
31 endmodule
32
```

2X1 MUX:

Project Summary × carryskip.v × ripplecarryadder.v × fulladder.v × mux2by1.v × propg.v ×

C:/Users/jenet/projectinternshipfinal/projectinternshipfinal.srscs/sources_1/new/mux2by1.v

Q

19

//

20

////////////////////////////////////

21

22

module mux2by1(I0,I1,sel,out);

23

24

input I0,I1,sel;

25

output reg out;

26

27

always @(*) begin

28

if(sel)

29

out=I1;

30

else

31

out=I0;

32

end

33

endmodule

4 BIT D FLIP FLOP:


carryskip.v × ripplecarryadder.v × fulladder.v × mux2by1.v × propg.v × dff4.v × dff.v

C:/Users/jenet/projectinternshipfinal/projectinternshipfinal.srscs/sources_1/new/dff4.v

Q


```
21
22 module dff4(out,out_b,in,clk,clear);
23
24 input [3:0]in;
25 input clk,clear;
26 output reg [4:0]out,out_b;
27
28 always @(posedge clk or negedge clear)
29
30 if (clear==0)
31 begin
32 out=4'b0000;
33 out_b=4'b1111;
34 end
35 else
36 begin
37 out<=in;
38 out_b<=~in;
39 end
40
41 endmodule
```

1 BIT D FLIP FLOP:

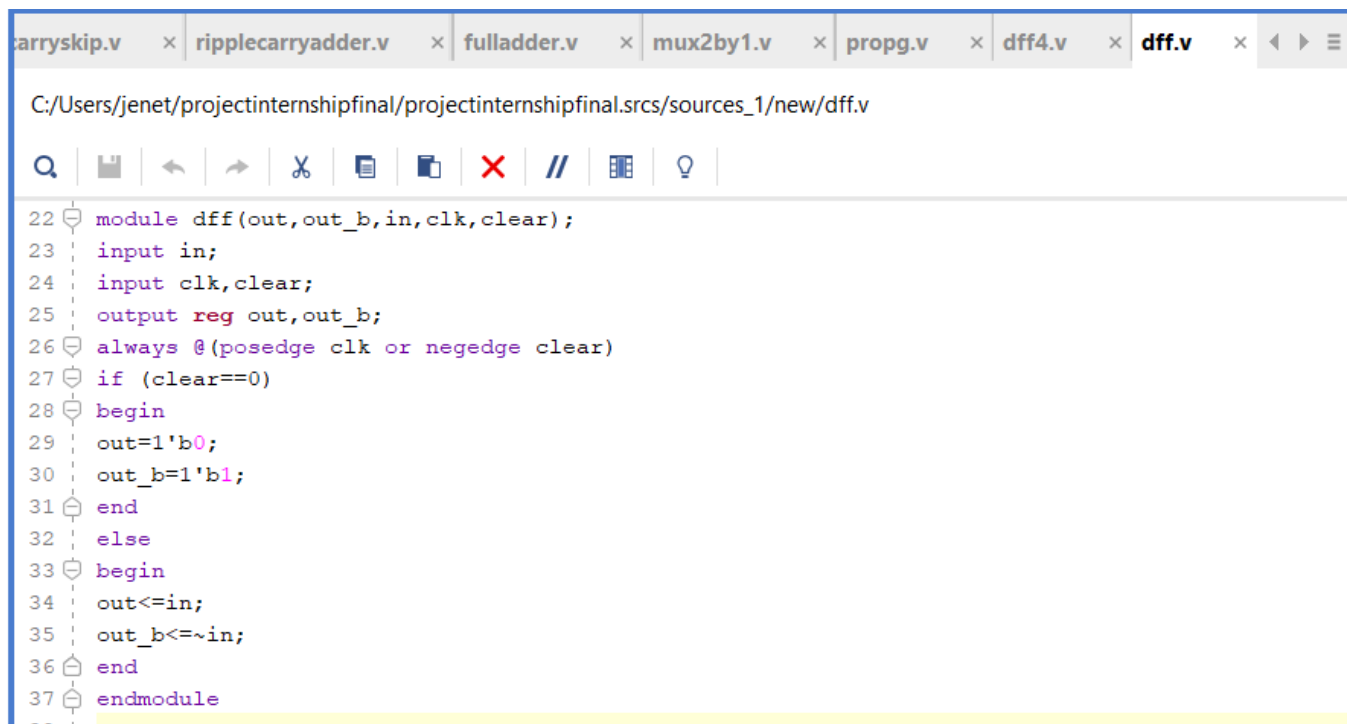

```
22 module dff(out,out_b,in,clk,clear);
23   input in;
24   input clk,clear;
25   output reg out,out_b;
26   always @(posedge clk or negedge clear)
27   if (clear==0)
28   begin
29     out=1'b0;
30     out_b=1'b1;
31   end
32   else
33   begin
34     out<=in;
35     out_b<=~in;
36   end
37 endmodule
```

TOP MODULE:

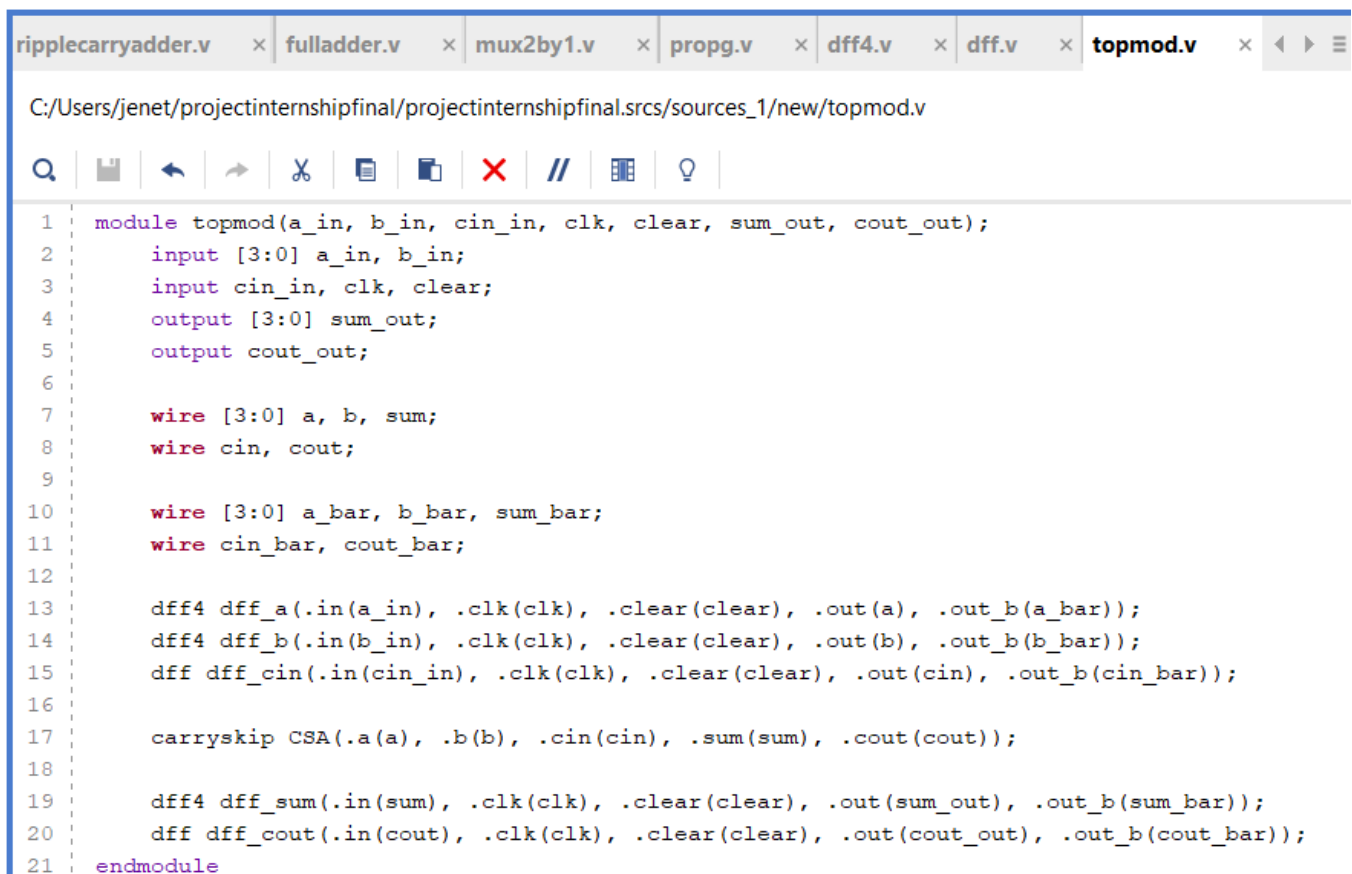

```
1 module topmod(a_in, b_in, cin_in, clk, clear, sum_out, cout_out);
2   input [3:0] a_in, b_in;
3   input cin_in, clk, clear;
4   output [3:0] sum_out;
5   output cout_out;
6
7   wire [3:0] a, b, sum;
8   wire cin, cout;
9
10  wire [3:0] a_bar, b_bar, sum_bar;
11  wire cin_bar, cout_bar;
12
13  dff4 dff_a(.in(a_in), .clk(clk), .clear(clear), .out(a), .out_b(a_bar));
14  dff4 dff_b(.in(b_in), .clk(clk), .clear(clear), .out(b), .out_b(b_bar));
15  dff dff_cin(.in(cin_in), .clk(clk), .clear(clear), .out(cin), .out_b(cin_bar));
16
17  carryskip CSA(.a(a), .b(b), .cin(cin), .sum(sum), .cout(cout));
18
19  dff4 dff_sum(.in(sum), .clk(clk), .clear(clear), .out(sum_out), .out_b(sum_bar));
20  dff dff_cout(.in(cout), .clk(clk), .clear(clear), .out(cout_out), .out_b(cout_bar));
21 endmodule
```

UTILIZATION AREA SUMMARY:

Tcl ConsoleMessagesLogReportsDesign RunsDRCMethodologyPowerTimingUtilization

Hierarchy

Hierarchy

Summary

Slice Logic

Slice LUTs (<1%)

LUT as Logic (<1%)

Slice Registers (<1%)

Register as Flip Flop (<1%)

Slice Logic Distribution

Slice (<1%)

SLICEL

Slice Registers (<1%)

Register driven from w

Name

1

Slice LUTs

(32600)

Slice Registers

(65200)

Slice

(8150)

LUT as Logic

(32600)

Bonded IOB

(210)

BUFGCTRL

(32)

topmod

6

14

4

6

16

1

dff_a (dff4)

4

4

4

4

0

0

dff_b (dff4_0)

1

4

3

1

0

0

dff_cin (dff)

1

1

2

1

0

0

dff_cout (dff_1)

0

1

1

0

0

0

dff_sum (dff4_2)

0

4

2

0

0

0

utilization_1

TIMING REPORT:

Tcl ConsoleMessagesLogReportsDesign RunsDRCMethodologyPowerTiming

Design Timing Summary

General Information

Timer Settings

Design Timing Summary

Clock Summary (1)

Methodology Summary (14)

Check Timing (15)

Intra-Clock Paths

Inter-Clock Paths

Other Path Groups

User Ignored Paths

Unconstrained Paths

Setup

Worst Negative Slack (WNS): 7.931 ns

Total Negative Slack (TNS): 0.000 ns

Number of Failing Endpoints: 0

Total Number of Endpoints: 5

Hold

Worst Hold Slack (WHS): 0.149 ns

Total Hold Slack (THS): 0.000 ns

Number of Failing Endpoints: 0

Total Number of Endpoints: 5

Pulse Width

Worst Pulse Width Slack (WPWS): 4.500 ns

Total Pulse Width Negative Slack (TPWS): 0.000 ns

Number of Failing Endpoints: 0

Total Number of Endpoints: 15

All user specified timing constraints are met.

Timing Summary - timing_1

TIMING CONSTRAINTS:

yskip.vripplecarryadder.vfulladder.vmux2by1.vpropg.vdff.vdff4.vTiming Constraints

Create Clock

Clocks (1)

Create Clock (1)

Create Generated Clock (0)

Rename Auto-Derived Clock (0)

Set Clock Latency (0)

Position

Clock Name

Period (ns)

Rise At (ns)

Fall At (ns)

Add Clock

Source Objects

Source File

Scoped Cell

1

clk

10.000

0.000

5.000

☒

clk

<unsaved co

Double click to create a Create Clock constraint

INTRA CLOCK PATHS:

Tcl ConsoleMessagesLogReportsDesign RunsDRCMethodologyPowerTiming

Intra-Clock Paths

Clock

Edges (WNS)

WNS (ns)

TNS (ns)

Failing Endpoints (TNS)

Total Endpoints (TNS)

Edges (WHS)

WHS (ns)

THS (ns)

Failing Endpoints (THS)

Total Endpoints (THS)

WPWS (ns)

TPWS (ns)

Failing Endpoints (TPWS)

Total Endpoints (TPWS)

clk

rise - rise

7.931

0.000

0

5

rise - rise

0.149

0.000

0

5

4.500

0.000

0

15

Timing Summary - timing_1

UNCONSTRAINED PATHS:

Tcl ConsoleMessagesLogReportsDesign RunsDRCMethodologyPowerTiming ×

Unconstrained Paths - NONE - clk

Clock Summary (1)
Methodology Summary (14)
Check Timing (15)
Intra-Clock Paths
clk
Inter-Clock Paths
Other Path Groups
User Ignored Paths
Unconstrained Paths
NONE to clk
Setup (10)
Hold (10)
clk to NONE

Group Name: (none)
From Clock:
To Clock: clk

Statistics

| Type | Total Endpoints |
|-----------|-----------------|
| Max Delay | 23 |
| Min Delay | 23 |

Timing Summary - timing_1

DELAYS:

Tcl ConsoleMessagesLogReportsDesign RunsDRCMethodologyPowerTiming ×

Check Timing

Clock Summary (1)
Methodology Summary (14)
Check Timing (15)
Intra-Clock Paths
clk
Inter-Clock Paths
Other Path Groups
User Ignored Paths
Unconstrained Paths
NONE to clk
Setup (10)
Hold (10)
clk to NONE

| Timing Check | Count | Worst Severity |
|----------------------------------|-------|----------------|
| no_input_delay | 10 | High |
| no_output_delay | 5 | High |
| no_clock | 0 | |
| constant_clock | 0 | |
| pulse_width_clock | 0 | |
| unconstrained_internal_endpoints | 0 | |
| multiple_clock | 0 | |
| generated_clocks | 0 | |
| loops | 0 | |
| partial_input_delay | 0 | |
| partial_output_delay | 0 | |

Timing Summary - timing_1

POWER REPORT:

Tcl ConsoleMessagesLogReportsDesign RunsDRCMethodologyPower × Timing

Summary

Settings
Summary (0.074 W, Margin: N/A)
Power Supply
Utilization Details
Hierarchical (0.003 W)
Clocks (<0.001 W)
Signals (<0.001 W)
Data (<0.001 W)
Set/Reset (0 W)
Logic (<0.001 W)
I/O (0.003 W)

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.074 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 25.4°C
Thermal Margin: 59.6°C (12.0 W)
Ambient Temperature: 25.0 °C
Effective θJA: 4.9°C/W
Power supplied to off-chip devices: 0 W

On-Chip Power

Dynamic: 0.003 W (5%)
Clocks: <0.001 W (14%)
Signals: <0.001 W (2%)
Logic: <0.001 W (1%)
I/O: 0.003 W (83%)
Device Static: 0.070 W (95%)

power_1

CARRY SELECT ADDER REPORT

NAME: DHARSHAN S

GMAIL: dhmarshans640@gmail.com

CARRY SELECT ADDER CODE:

```
Project Summary x toptop.v x fulladderbase.v x carryselect.v x ddddselect.v x dselect.v x < > ≡ ? □ ↗
K:/XILINX/INTERNSHIP_REPORT1/INTERNSHIP_REPORT1.srscs/sources_1/new/carryselect.v
🔍 📁 ⬅ ➡ ✂ 📄 📋 ✖ // 📊 💡 ⚙
1 module carryselect(output [3:0] sum0,sum1, reg [3:0] sum,output c_out,
2 input [3:0] a, b,c_in);
3 wire c1_0, c2_0, c3_0, cout_0;
4 wire c1_1, c2_1, c3_1, cout_1;
5
6 FULL_ADDER FA1(sum0[0], c1_0, a[0], b[0], c_in);
7 FULL_ADDER FA2(sum0[1], c2_0, a[1], b[1], c1_0);
8 FULL_ADDER FA3(sum0[2], c3_0, a[2], b[2], c2_0);
9 FULL_ADDER FA4(sum0[3], cout_0, a[3], b[3], c3_0);
10
11 FULL_ADDER FA5(sum1[0], c1_1, a[0], b[0], c_in);
12 FULL_ADDER FA6(sum1[1], c2_1, a[1], b[1], c1_1);
13 FULL_ADDER FA7(sum1[2], c3_1, a[2], b[2], c2_1);
14 FULL_ADDER FA8(sum1[3], cout_1, a[3], b[3], c3_1);
15
16 always @(*) begin
17 case(c_in)
18 1'b0: sum = sum0;
19 1'b1: sum = sum1;
20 endcase
21 end
22 assign c_out = (c_in == 1'b0) ? cout_0 : cout_1;
23 endmodule
24
```

ONE BIT ADDER:


```
fulladderbase.v x carryselect.v x ddddselect.v x dselect.v x Untitled 1 x carrysele < > ≡ ? □ ↗
K:/XILINX/INTERNSHIP_REPORT1/INTERNSHIP_REPORT1.srscs/sources_1/new/fulladderbase.v
🔍 📁 ⬅ ➡ ✂ 📄 📋 ✖ // 📊 💡 ⚙
1 module fulladderbase(sum,c_out,a,b,c_in);
2 input a,b,c_in;
3 output reg [3:0]sum;
4 output reg c_out;
5
6 always @(*)
7 begin
8 sum=a^b^c_in;
9 c_out=(a&b) | (b&c_in) | (a&c_in);
10 end
11 endmodule
12
```

TEST BENCH:

```
ase.v x carryselect.v x ddddselect.v x dselect.v x Untitled 1 x carryselecttb.v x
K:/XILINX/INTERNSHIP_REPORT1/INTERNSHIP_REPORT1.srscs/sim_1/new/carryselecttb.v

3 module FULL_ADDER_4BIT_TB;
4     reg [3:0] a, b;
5     reg c_in;
6     wire [3:0] sum;
7     wire c_out;
8     wire c1, c2, c3;
9
10    carryselect uut(.sum0(sum0),.sum1(sum1),.sum(sum),.c_out(c_out),.a(a),.b(b),.c_in(
11
12    initial begin
13
14        a = 4'b1011; b = 4'b0100; c_in = 0; #10;
15        a = 4'b1011; b = 4'b0100; c_in = 1; #10;
16        a = 4'b0011; b = 4'b1000; c_in = 0; #10;
17        a = 4'b0011; b = 4'b1000; c_in = 1; #10;
18        $finish;
19    end
20
21 endmodule
22
```

WAVEFORM:

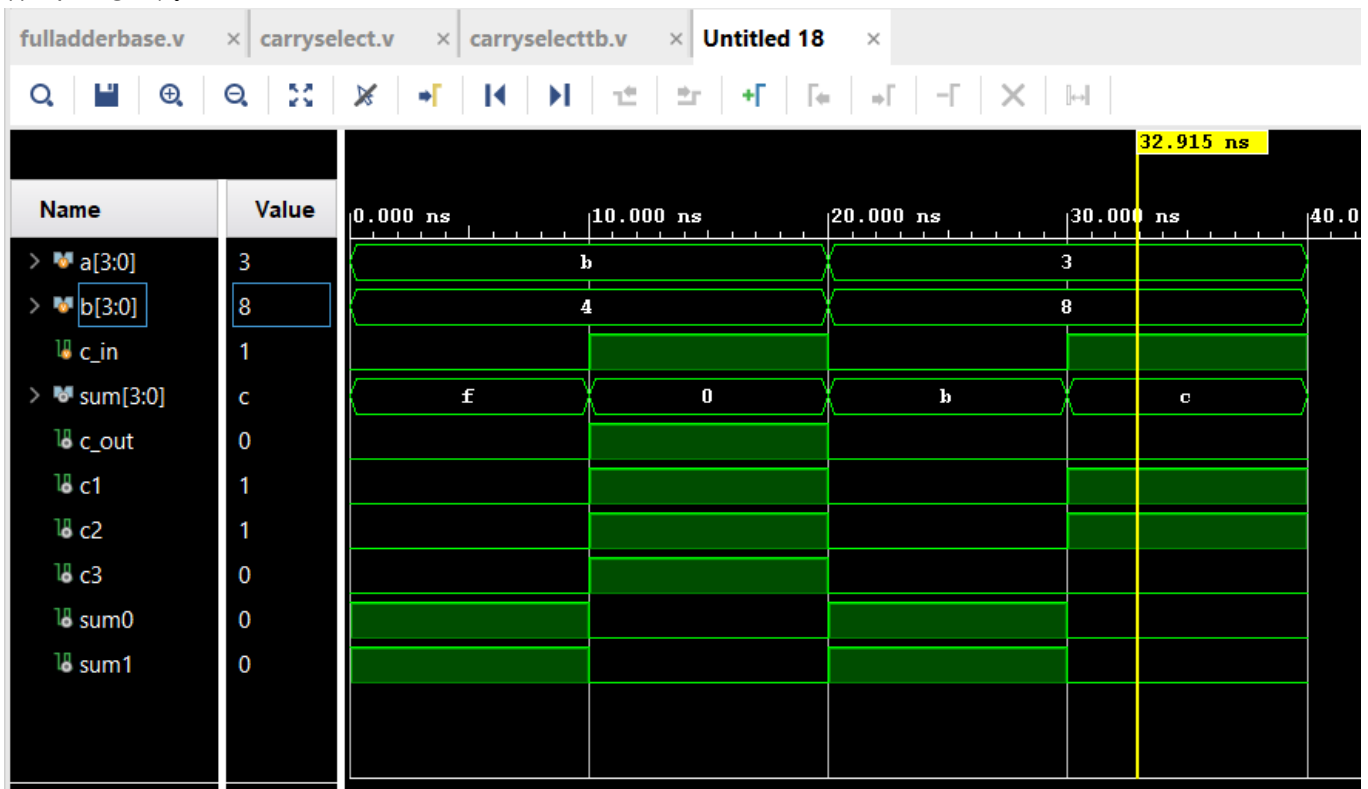

ONE BIT D FLIPFLOP:

Project Summary x FULLADDERFUNC.v x dselect.v x toptop.v x ddddselect.v

K:/XILINX/INTERNSHIP_REPORT1/INTERNSHIP_REPORT1.srcs/sources_1/new/dselect.v

```
1 module D_FF_1BIT (  
2     input clk1,  
3     input reset1,  
4     input d,  
5     output reg q,  
6     output reg qb  
7 );  
8  
9     always @(posedge clk1 or posedge reset1)  
10    begin  
11        if (reset1)  
12            begin  
13                q <= 1'b0;  
14                qb<=1'b1;  
15            end  
16        else  
17            begin  
18                q <= d;  
19                qb <= ~d;  
20            end  
21        end  
22    end  
23 endmodule
```

FOUR BIT D FLIPFLOP:

Project Summary x FULLADDERFUNC.v x dselect.v x toptop.v x ddddselect.v *

K:/XILINX/INTERNSHIP_REPORT1/INTERNSHIP_REPORT1.srcs/sources_1/new/dddselect.v

```
1 module D_FF_4BIT (input clk,input reset,input [3:0] d,  
2     output reg [3:0] q,output reg [3:0] qb);  
3     always @(posedge clk or posedge reset)  
4     begin  
5         if (reset)  
6             begin  
7                 q <= 4'b0000;  
8                 qb<=4'b1111; // Reset output to 0  
9             end  
10        else  
11            begin  
12                q <= d;  
13                qb <= ~d;  
14            end  
15        end  
16    end  
17 endmodule
```

TOPMODULE:

immary x Device x dselect.v x toptop.v x ddddselect.v x carryselect.v x

K:/XILINX/INTERNSHIP_REPORT1/INTERNSHIP_REPORT1.srscs/sources_1/new/toptop.v

Q

📁

↶

↷

✂

📄

📄

✖

//

📊

💡

1

module fourtop(a_in, b_in, cin_in, clk, clear, sum_out, cout_out);

2

input [3:0] a_in, b_in;

3

input cin_in, clk, clear;

4

output [3:0] sum_out;

5

output cout_out;

6

7

wire [3:0] a, b, sum, sumzer, sumone;

8

wire cin, cout;

9

wire [3:0] a_bar, b_bar, sum_bar;

10

wire cin_bar, cout_bar;

11

12

D_FF_4BIT dff_a(clk, clear, a_in, a, a_bar);

13

D_FF_4BIT dff_b(clk, clear, b_in, b, b_bar);

14

D_FF_1BIT dff_c(clk, clear, cin_in, cin, cin_bar);

15

16

carryselect FA1(sumzer, sumone, sum, cout, a, b, cin);

17

18

D_FF_4BIT dff_sum(clk, clear, sum, sum_out, sum_bar);

19

D_FF_1BIT dff_cout(clk, clear, cout, cout_out, cout_bar);

20

endmodule

21

UTILIZATION AREA SUMMARY:

| Name | 1 | Slice LUTs (32600) | Slice Registers (65200) | Bonded IOB (210) | BUFGCTRL (32) |
|------------------------|---|-----------------------|----------------------------|---------------------|------------------|
| fourtop | | 11 | 14 | 16 | 1 |
| dff_a (D_FF_4BIT) | | 7 | 4 | 0 | 0 |
| dff_b (D_FF_4BIT_0) | | 4 | 4 | 0 | 0 |
| dff_c (D_FF_1BIT) | | 0 | 1 | 0 | 0 |
| dff_cout (D_FF_1BIT_1) | | 0 | 1 | 0 | 0 |
| dff_sum (D_FF_4BIT_2) | | 0 | 4 | 0 | 0 |

TIMING REPORTS :

| Design Timing Summary | | | | | |
|--|--|----------------------------------|--|---|--|
| Setup | | Hold | | Pulse Width | |
| Worst Negative Slack (WNS): 8.083 ns | | Worst Hold Slack (WHS): 0.131 ns | | Worst Pulse Width Slack (WPWS): 4.500 ns | |
| Total Negative Slack (TNS): 0.000 ns | | Total Hold Slack (THS): 0.000 ns | | Total Pulse Width Negative Slack (TPWS): 0.000 ns | |
| Number of Failing Endpoints: 0 | | Number of Failing Endpoints: 0 | | Number of Failing Endpoints: 0 | |
| Total Number of Endpoints: 5 | | Total Number of Endpoints: 5 | | Total Number of Endpoints: 15 | |
| All user specified timing constraints are met. | | | | | |

TIMING CONSTRAINTS:

Create Clock

| Position | Clock Name | Period (ns) | Rise At (ns) | Fall At (ns) | Add Clock | Source Objects | Source File | Scoped Cell | Current Instance |
|----------|------------|-------------|--------------|--------------|-------------------------------------|----------------|------------------------|-------------|------------------|
| 1 | clk | 10.000 | 0.000 | 5.000 | <input checked="" type="checkbox"/> | clk | SYNTHESIS REPORT 1.xdc | | |

Double click to create a Create Clock constraint

INTRA CLOCK PATHS:

Intra-Clock Paths

| Clock | Edges (WNS) | WNS (ns) | TNS (ns) | Failing Endpoints (TNS) | Total Endpoints (TNS) | Edges (WHS) | WHS (ns) | THS (ns) | Failing Endpoints (THS) | Total Endpoints (THS) | WPWS (ns) | TPWS (ns) | Failing Endpoints (TPWS) | Total Endpoints (TPWS) |
|-------|-------------|----------|----------|-------------------------|-----------------------|-------------|----------|----------|-------------------------|-----------------------|-----------|-----------|--------------------------|------------------------|
| clk | rise - rise | 8.083 | 0.000 | 0 | 5 | rise - rise | 0.131 | 0.000 | 0 | 5 | 4.500 | 0.000 | 0 | 15 |

UNCONSTRAINED PATHS:

Unconstrained Paths - clk - NONE

Group Name: (none)

From Clock: clk

To Clock:

Statistics

| Type | Total Endpoints |
|-----------|-----------------|
| Max Delay | 5 |
| Min Delay | 5 |

Unconstrained Paths - NONE - clk

Group Name: (none)

From Clock:

To Clock: clk

Statistics

| Type | Total Endpoints |
|-----------|-----------------|
| Max Delay | 23 |
| Min Delay | 23 |

DELAY :

Check Timing


| Timing Check | Count <div>▼ 1</div> | Worst Severity |
|----------------------------------|----------------------|------------------|
| no_input_delay | 10 | <div></div> High |
| no_output_delay | 5 | <div></div> High |
| no_clock | 0 | |
| constant_clock | 0 | |
| pulse_width_clock | 0 | |
| unconstrained_internal_endpoints | 0 | |
| multiple_clock | 0 | |
| generated_clocks | 0 | |
| loops | 0 | |
| partial_input_delay | 0 | |
| partial_output_delay | 0 | |
| latch_loops | 0 | |

POWER REPORT:

- Settings
- Summary (0.088 W, Margin: N/A)
- Power Supply
- Utilization Details
 - Hierarchical (0.007 W)
 - Clocks (0.001 W)
 - Signals (<0.001 W)
 - Data (<0.001 W)

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

| | |
|-----------------------|---------------|
| Total On-Chip Power: | 0.088 W |
| Design Power Budget: | Not Specified |
| Process: | typical |
| Power Budget Margin: | N/A |
| Junction Temperature: | 25.2°C |

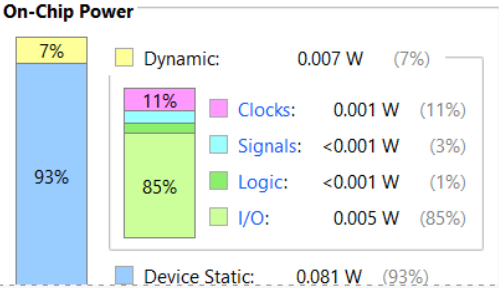

8 Conclusion

This project successfully compared four different adder architectures based on real synthesis reports.